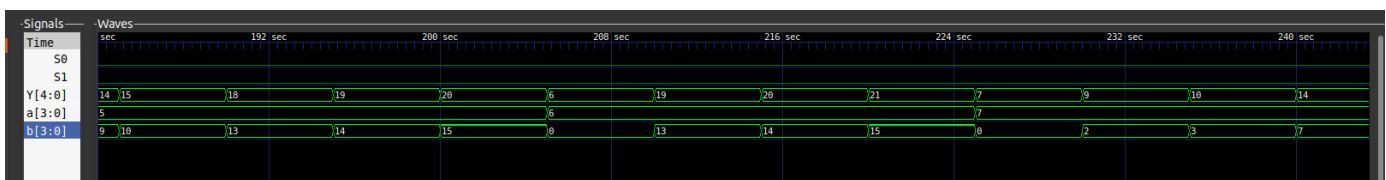


# VLSI PROJECT Report


E Druvitha, 2022102029

## VERILOG


S=00




S=01

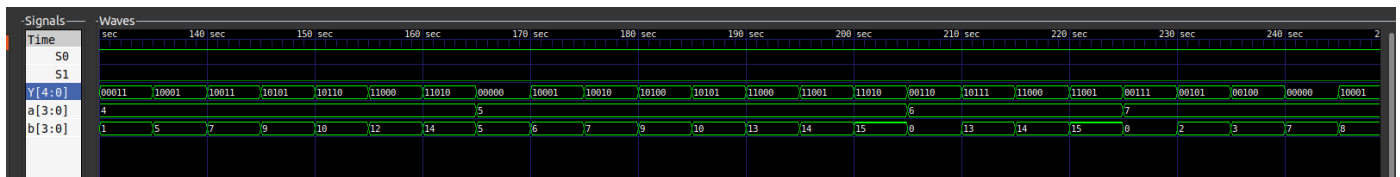

S=10

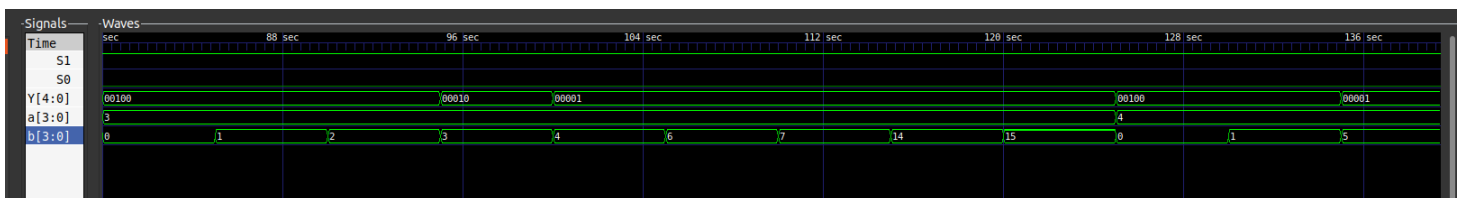

S = 11

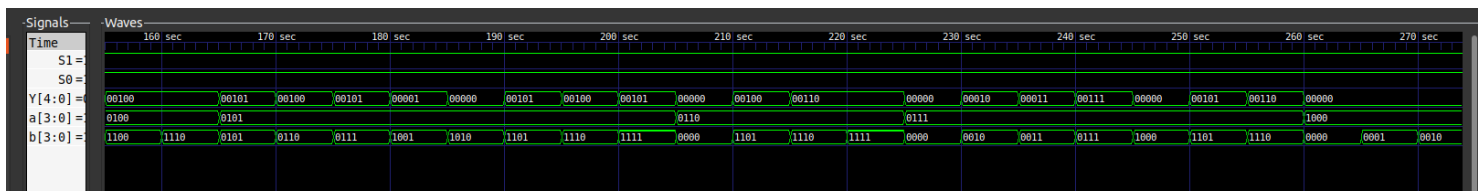

For comparator in the output y[2] represents a>b, y[1] represents a=b and y[0] represents b>a  
I.e if it is true the bit is 1 otherwise 0.

---


In SUBTRACTOR S = 01 the output is 5 bit sign representation.

For different type of inputs the outputs are plotted and attached above for different select lines.


---

## NGSPICE


S=00

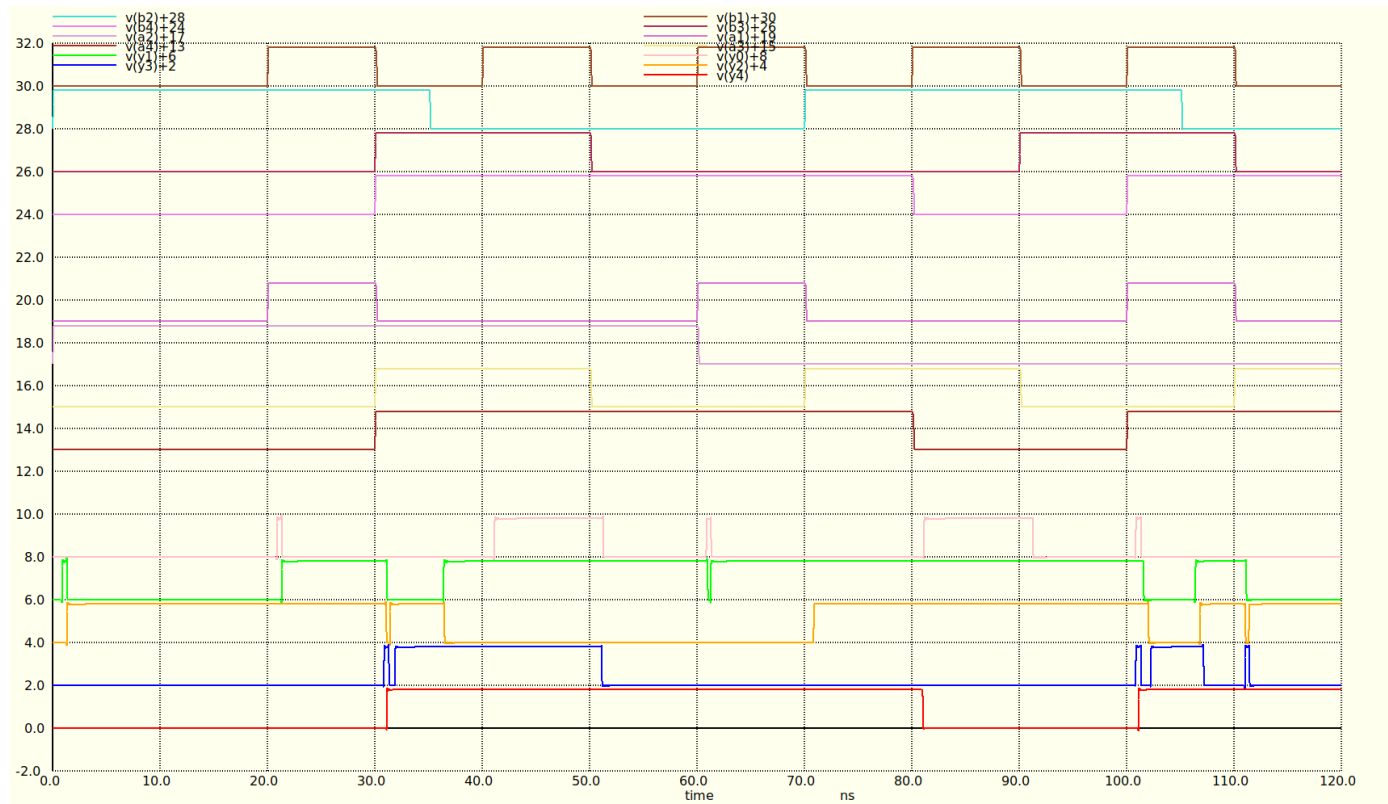


S=01

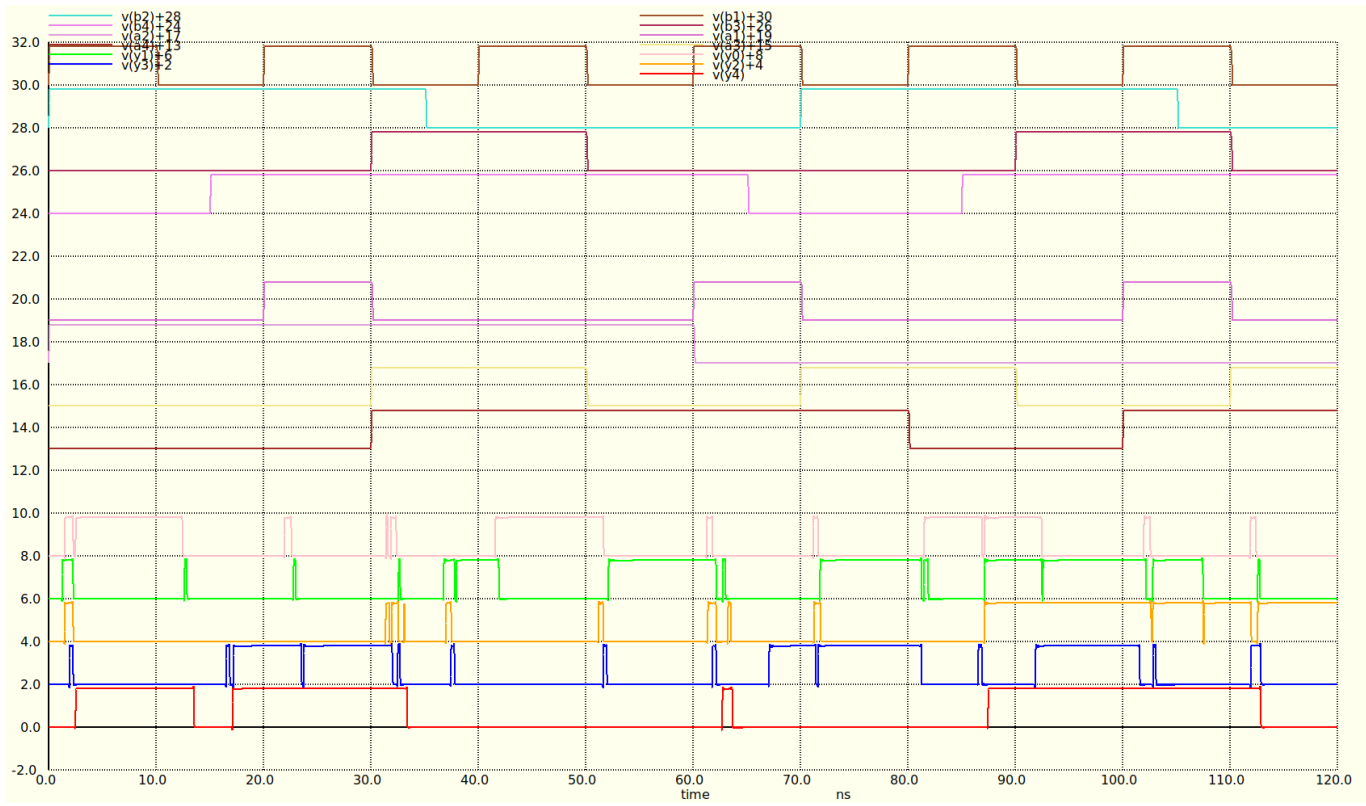

S = 10

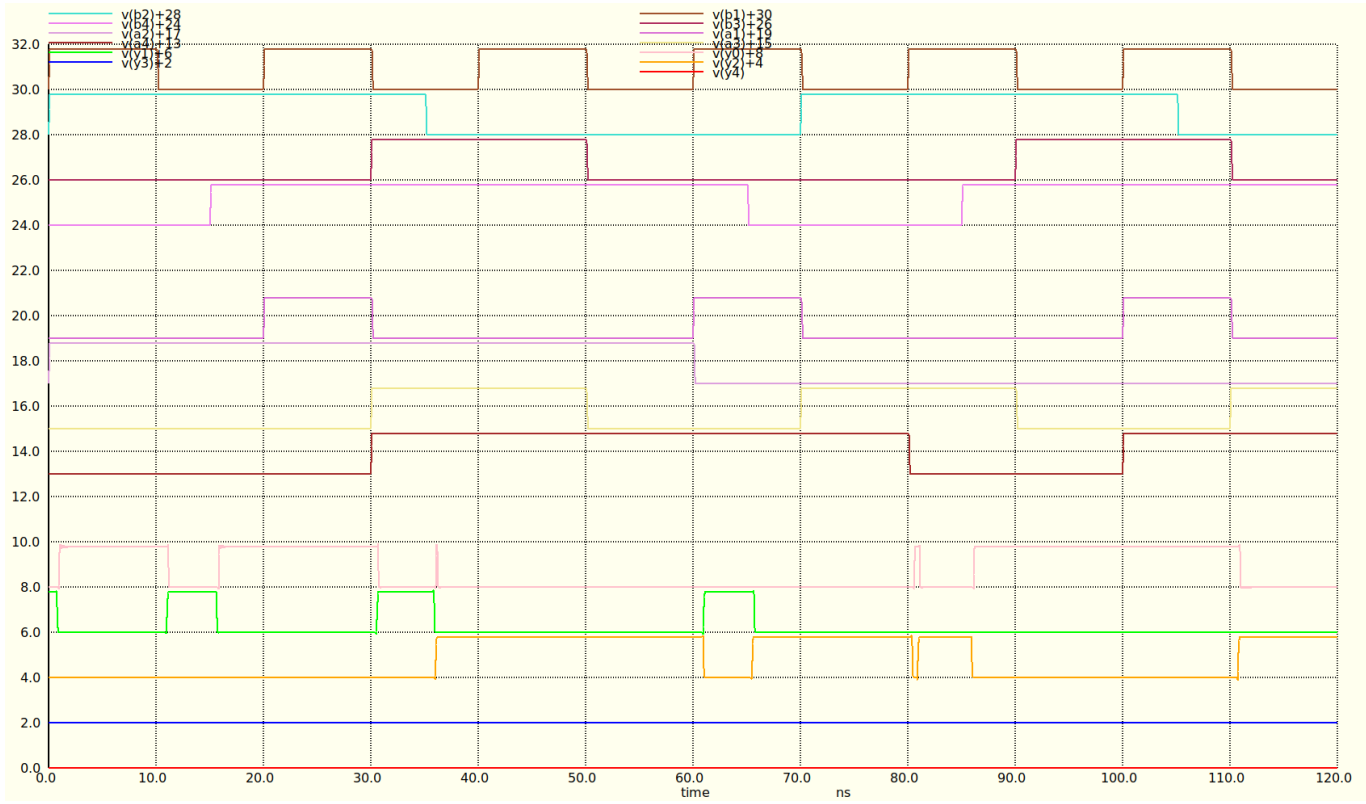


S = 11

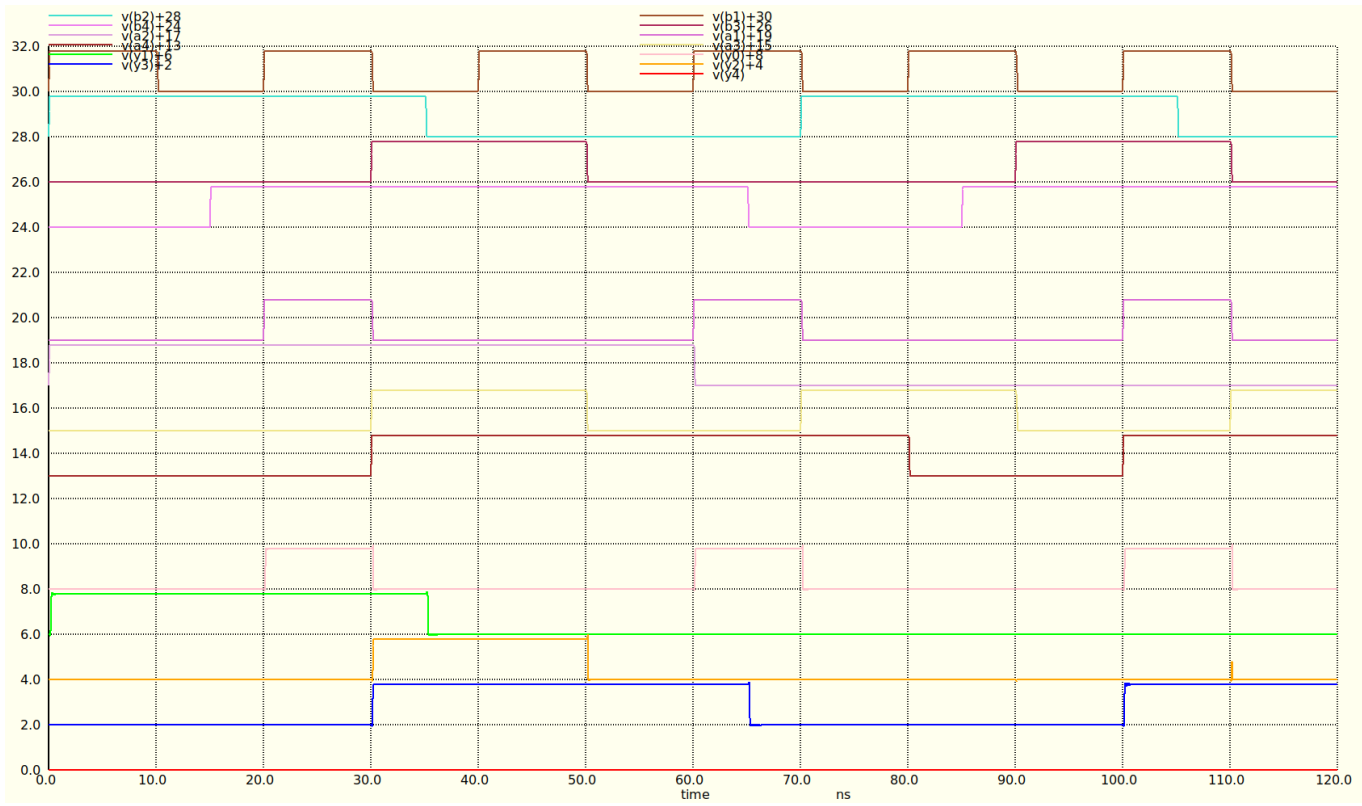


# MAGIC

Plots of outputs when extracted from layouts using ext2spice command line for different input lines  
Above 4 represents  $b[4:0]$ , next four represents  $a[4:0]$  and the bottom 5 represents output  $y[5:0]$   
Where the bottom line in each represents msb.


(i)  $S=00$

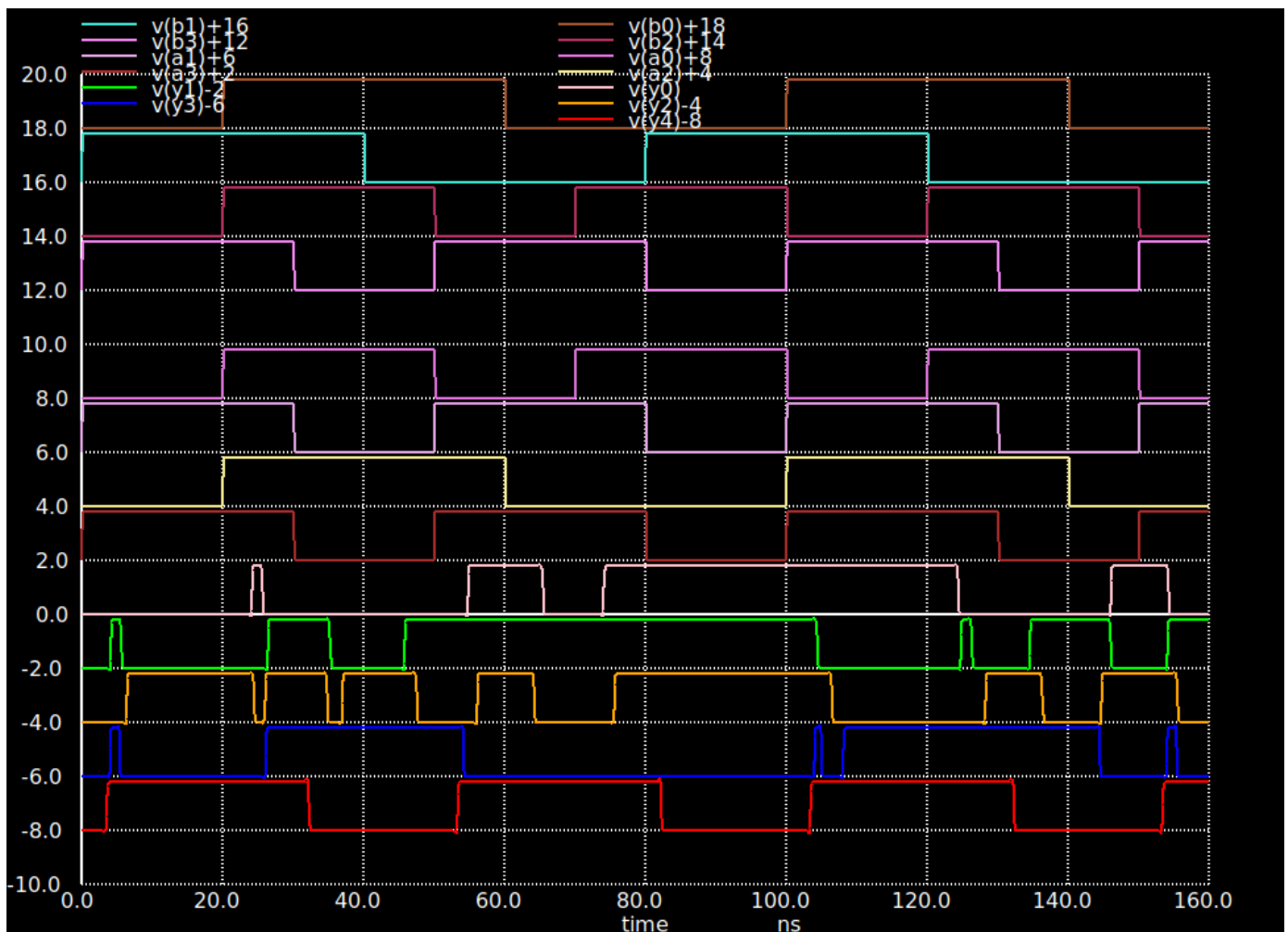

(ii)  $S = 01$

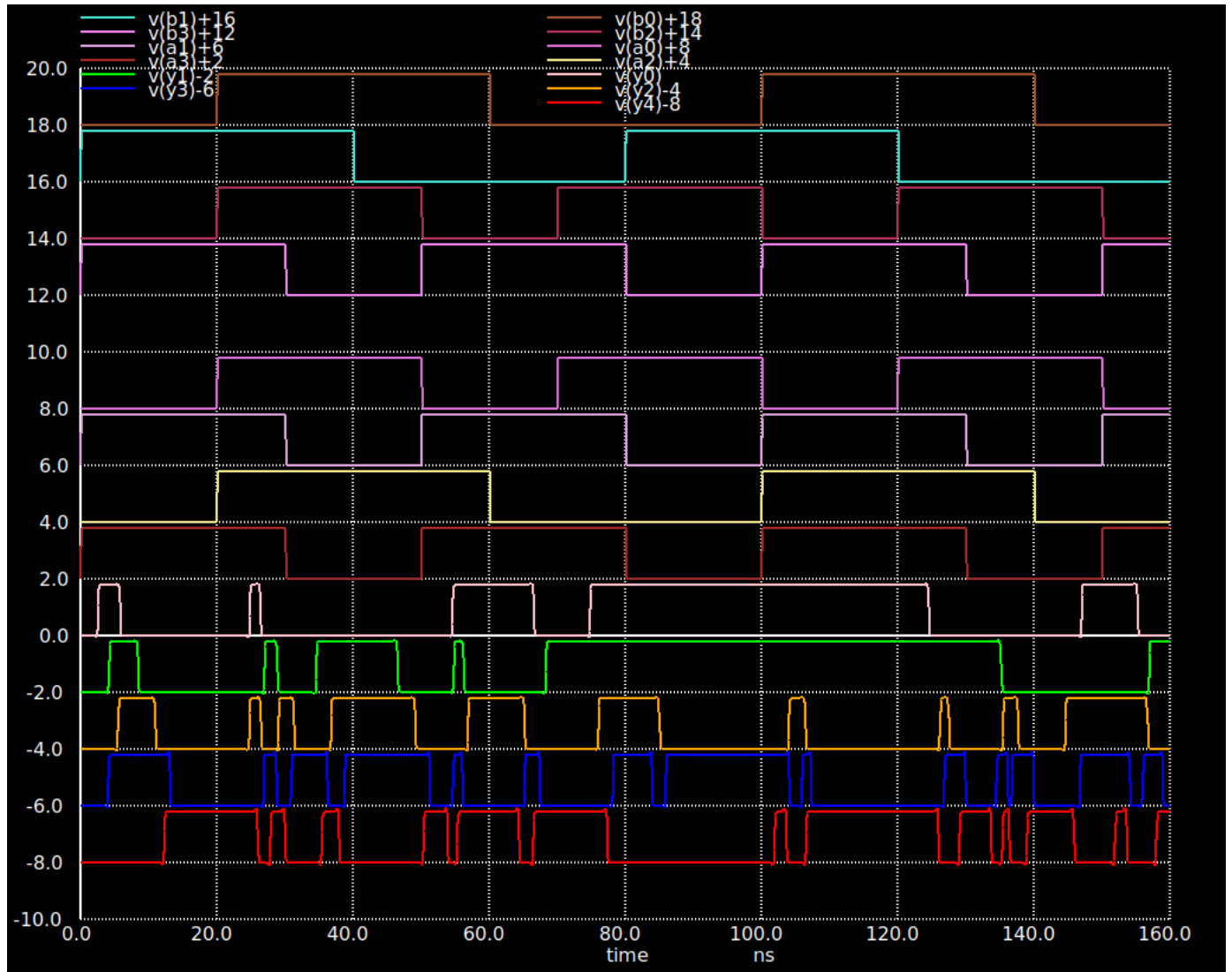


(iii)  $S = 10$

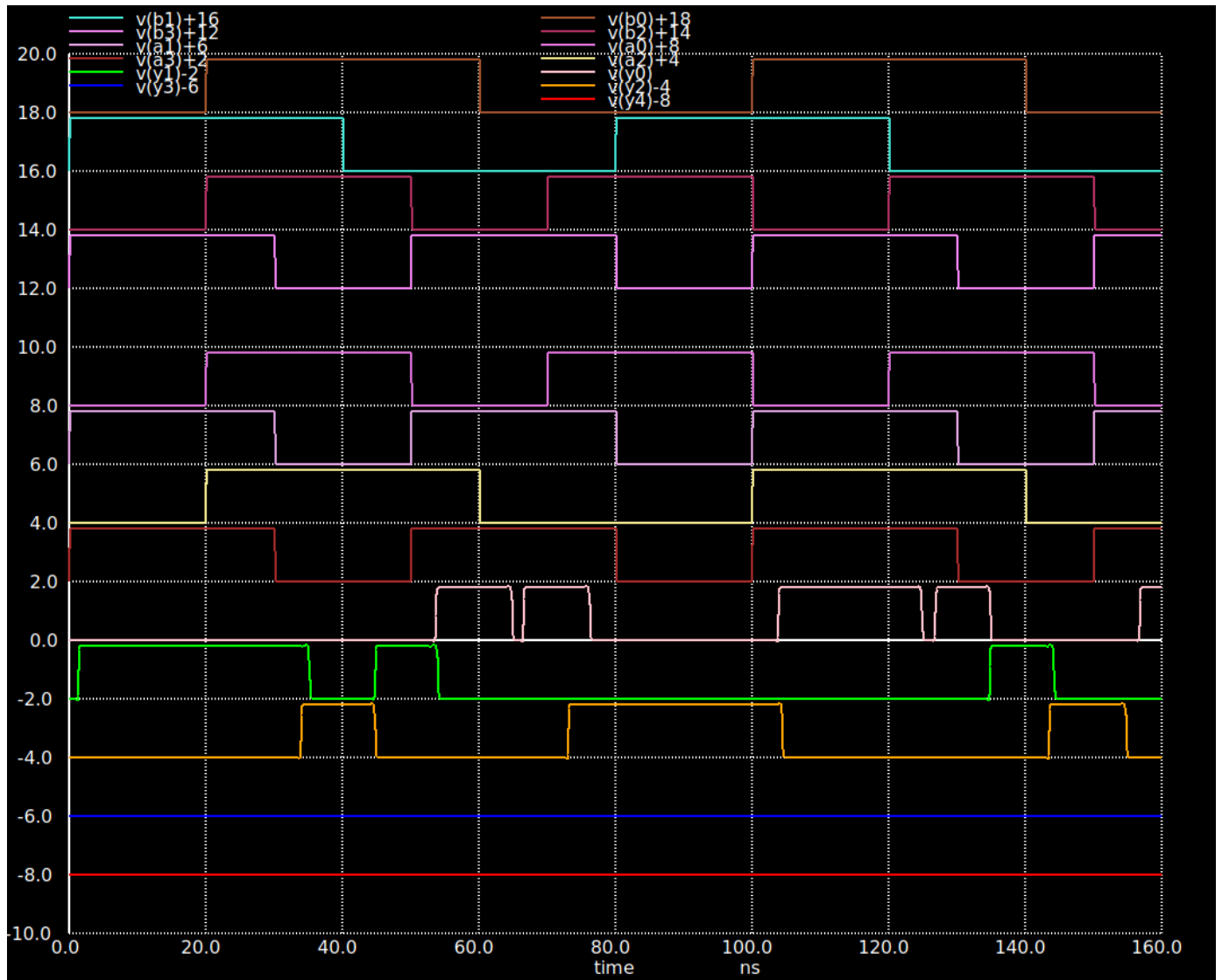




(iv)  $S = 11$

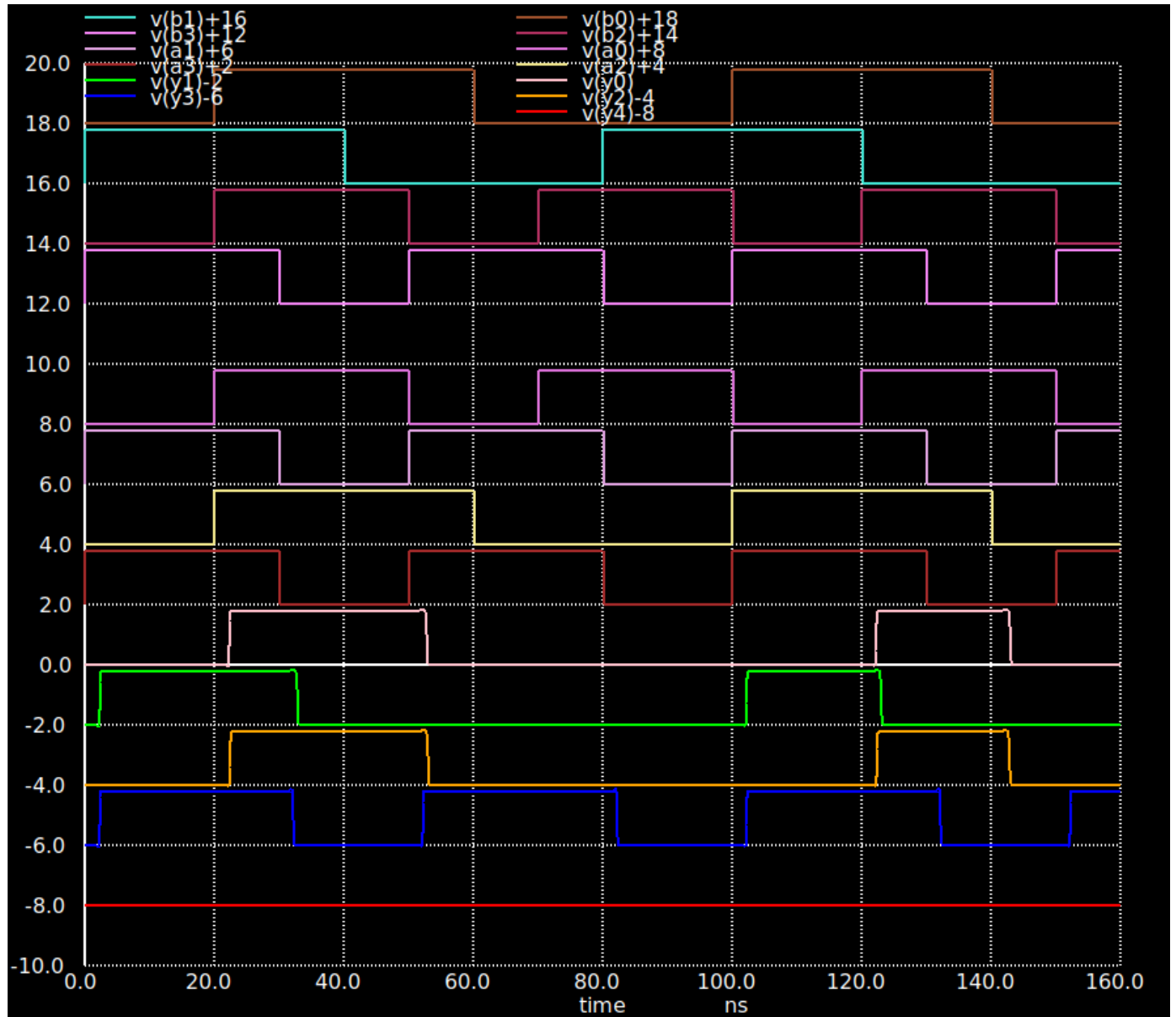

---


## Screenshots of magic layouts

### (i) Addsub part

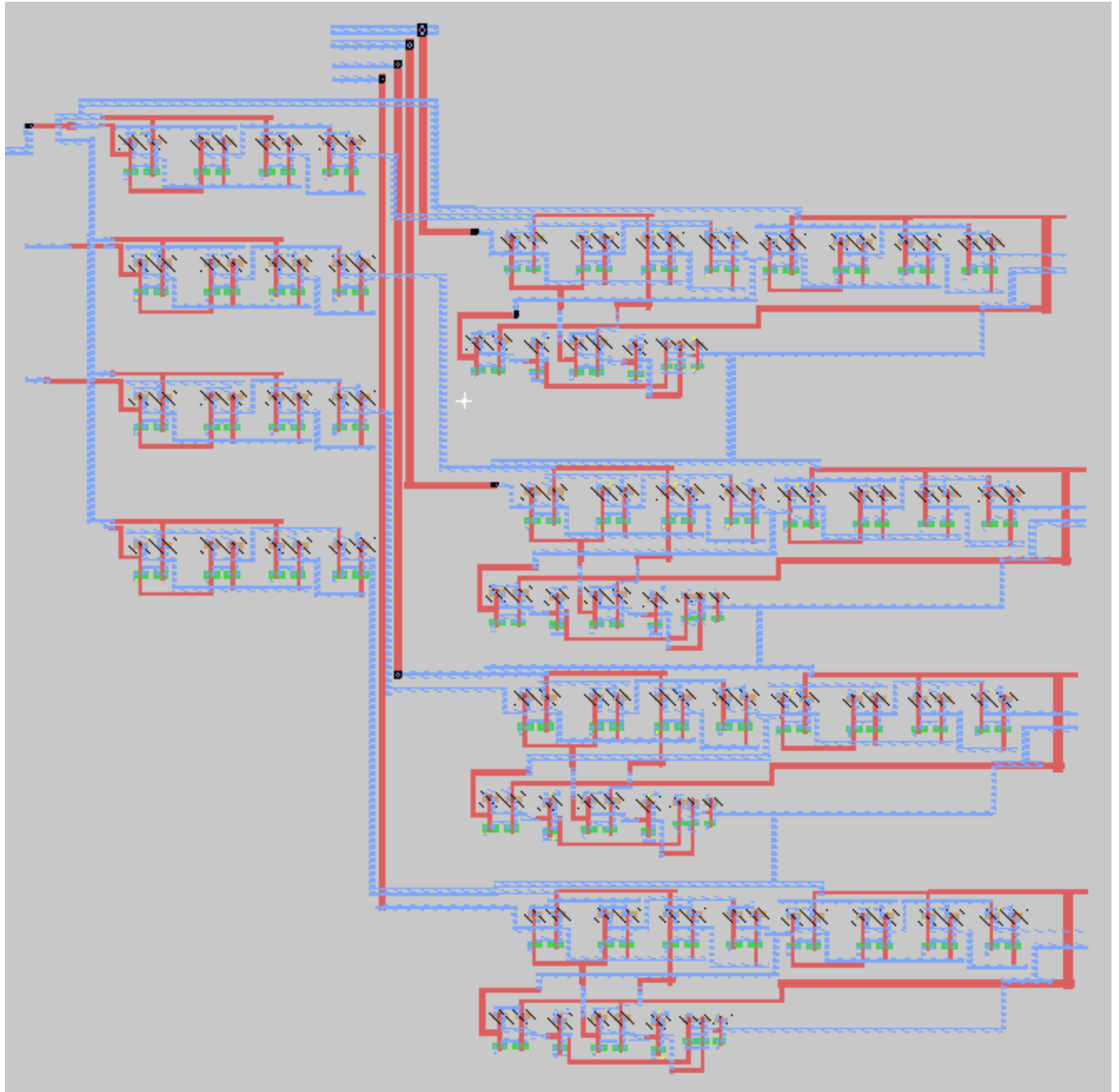


---

(ii) Comparator part

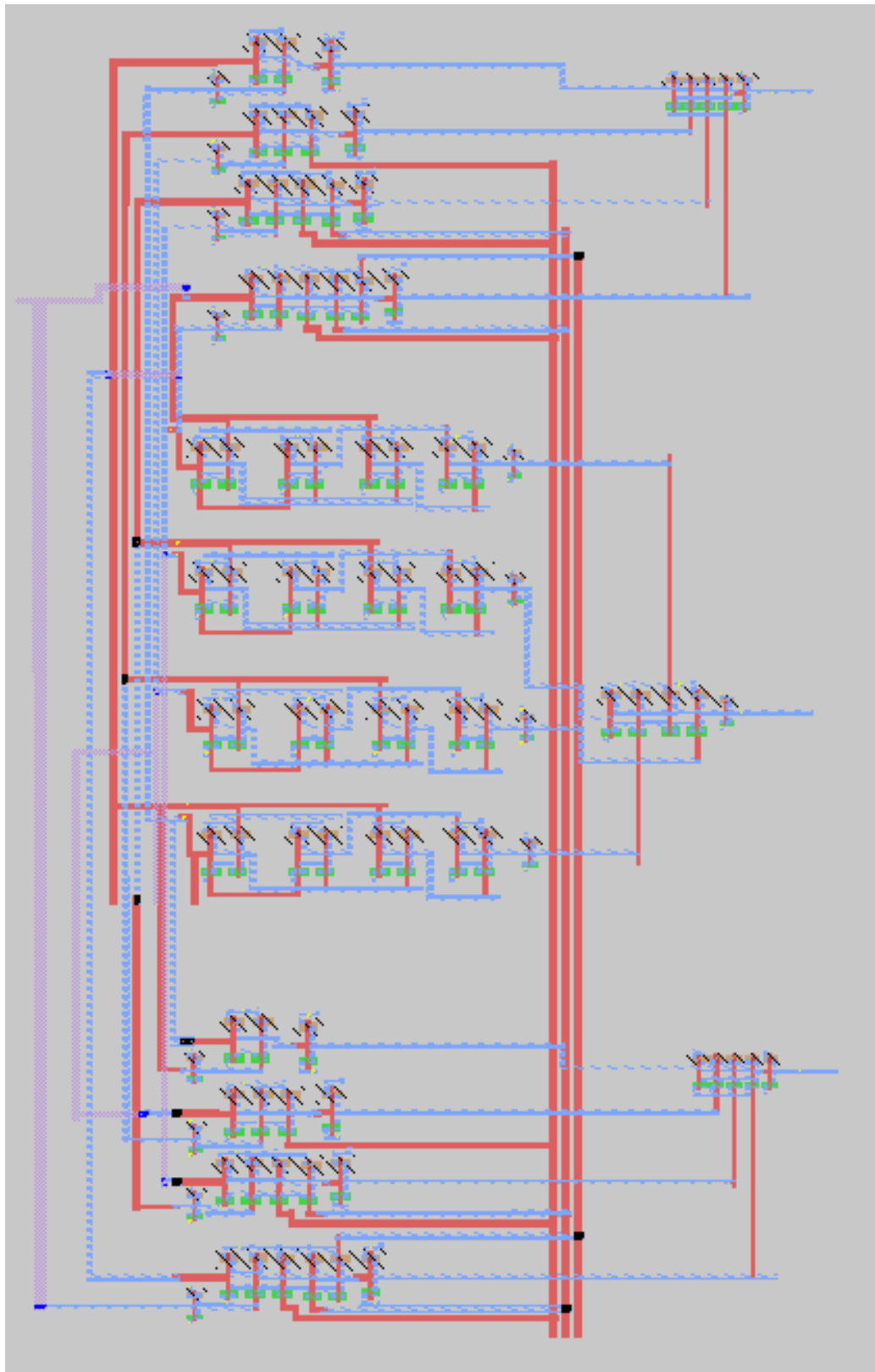


(iii) ANDing part

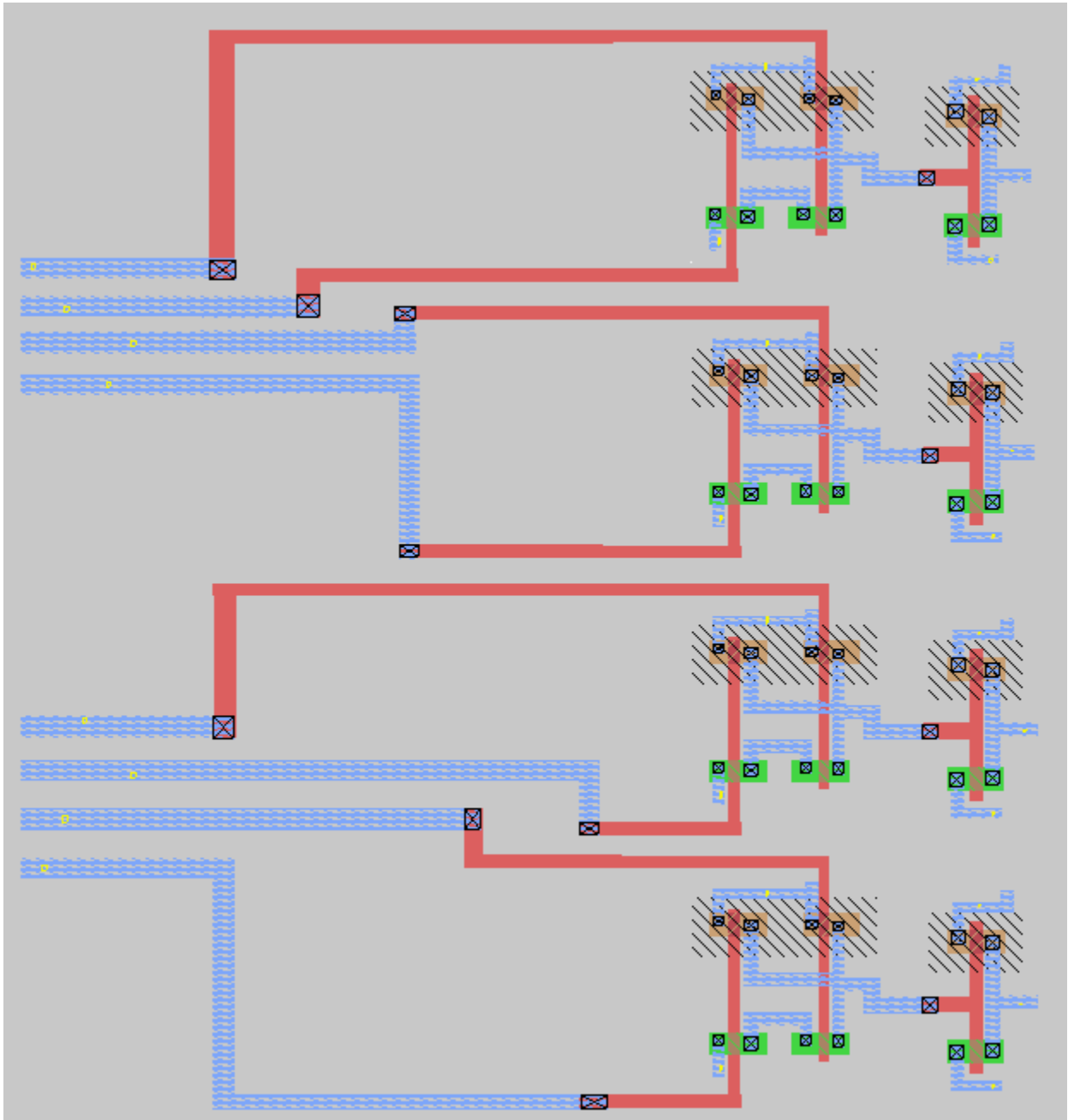

---

The total ALU part including mux

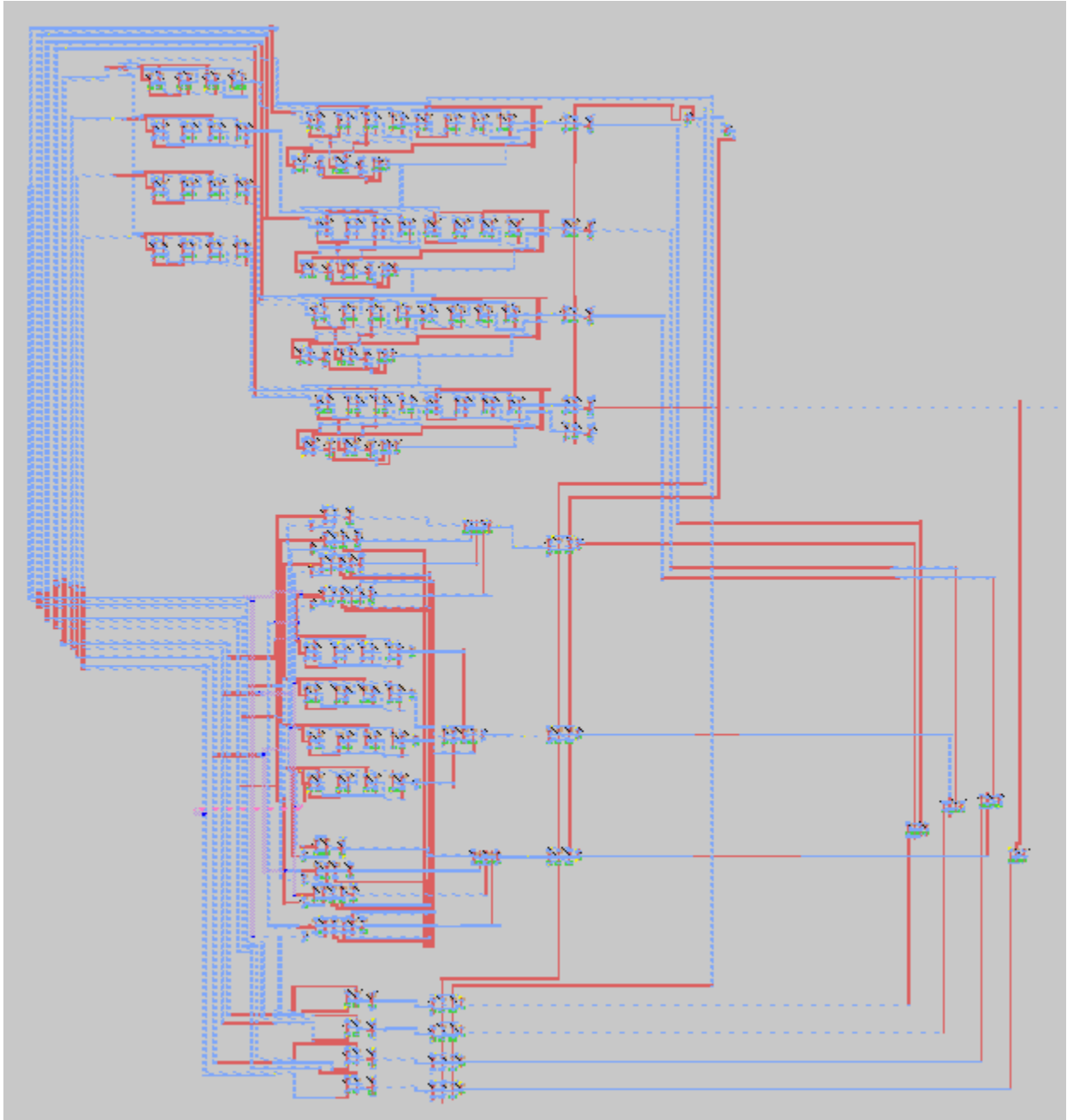

Using enable we implemented mux such that based on select lines output is displayed in spice when extracted from layout.

---

# Delay analysis

In a circuit the path between an input and an output with the maximum delay is known as Critical path.

## **ADDER :**

- For adder we have different cases to calculate delays
- We have 2 src files for delay analysis of input vs output for S = 00
- Src file 1 - adddel1 where we have inputs

A    1111 0000 1111 0000

B    0000 0000 0000 0000

Y    1111 0000 1111 0000

- Src file 2 - adddel2 where we have inputs

A    0000 0000 0000 0000

B    1111 0000 1111 0000

Y    1111 0000 1111 0000

- In src file1 we will get A vs Y delay i.e each a0,a1,a2,a3 vs each y0,y1,y2,y3 So total 16 delays and in src file2 we will get B vs Y delay Even 16 delays here So total of 32 delays in adder
- Now all these 32 delays are generated using python script and printed those delays in i1delay.txt
- Among the obtained delays the max delays are  
For y0 max delay is 5.43802e-09  
For y1 max delay is 5.39522e-09  
For y2 max delay is 5.49035e-09  
For y3 max delay is 5.20504e-09

---

## Subtractor:

- For the delay analysis of subtractor we do the same analysis as adder part but for different input cases and we have different src files named subdel1 and subdel2
- Here all the 32 delays are generated using python script and printed them in i2delay.txt.
- Among the obtained delays the max delays are

For y0 max delay is 4.98614e-09

For y1 max delay is 3.76208e-08

For y2 max delay is 3.89412e-08

For y3 max delay is 3.99361e-08

## Comparator:

- For this part we have 4 src files where src file1 - has inputs

A 1111 0000 1111 0000

B 0000 1111 0000 1111

Y0 1 0 1 0

Y1 0 0 0 0

Y3 0 1 0 1

From this we get delay of A vs Y0 and A vs Y3 total of 4 + 4 = 8 delays

- In src file2 we have inputs

A 0000 1111 0000 1111

B 1111 0000 1111 0000

Y0 0 1 0 1

---

Y1 0 0 0 0

Y3 1 0 1 0

From this we get delay of B vs Y0 and B vs Y3 total of  $4 + 4 = 8$  delays

- In src file3 we have inputs

A 1111 0000 1111 0000

B 1111 1111 1111 1111

Y0 0 0 0 0

Y1 1 0 1 0

Y3 0 1 0 1

From this we get delay of A vs Y1 total of 4 delays

- In src file4 we have inputs

A 1111 1111 1111 1111

B 1111 0000 1111 0000

Y0 0 1 0 1

Y1 1 0 1 0

Y3 0 0 0 0

From this we get delay of B vs Y1 total of 4 delays

- So total  $8 + 8 + 4 + 4 = 24$  delays total fro comparator
- Using a python script we generated the delays and printed them in i3delay.txt.
  - Among the obtained delays the max delays are  
For y0 max delay is 5.40446e-08



---

For y1 max delay is 2.68862e-09

For y2 max delay is 5.38176e-08

## **ANDing:**

- For delay analyzing of this part we only have one src file which test all the delays a vs y and b vs y So total of 32 delays
- Inputs in src files is

A 1111 0000 1111 0000

B 1111 0000 1111 0000

Y 1111 0000 1111 0000

- Among the obtained delays the max delays are

For y0 max delay is 2.33564e-09

For y1 max delay is 2.36815e-09

For y2 max delay is 2.40550e-09

For y3 max delay is 2.12758e-09

Among all the maximum delay is 5.40446e-08